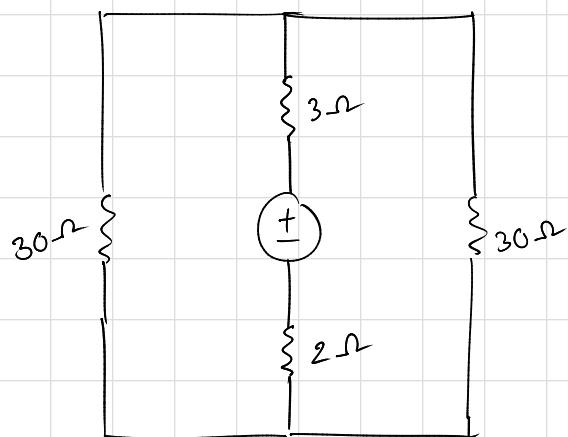


1. a)

$$14 + 20 \parallel (50 + 30)$$

$$= 30$$




$$12 + 27 \parallel (30 + 24)$$

$$= 30\Omega$$

$$2+3+30 \parallel 30$$


$$= 20$$

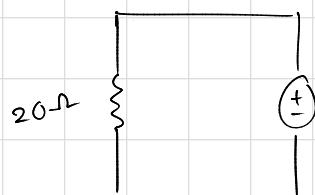

$$R_{eq} = 20\Omega$$

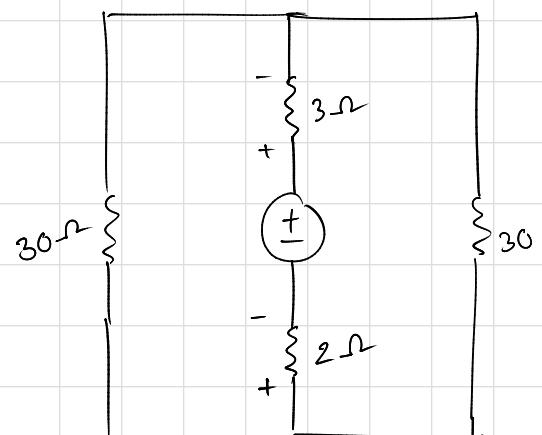b) voltage across 3Ω = $10 \times \frac{3}{2+3+30 \parallel 30} = 1.5V$

$\sim \sim \sim$ voltage across 2Ω = $10 \times \frac{2}{2+3+30 \parallel 30} = 1V$




c) current through the whole circuit

$$i = \frac{10}{20} = 0.5A$$

$$i_1 = 0.5 \times \frac{30}{30+30} = 0.25A$$
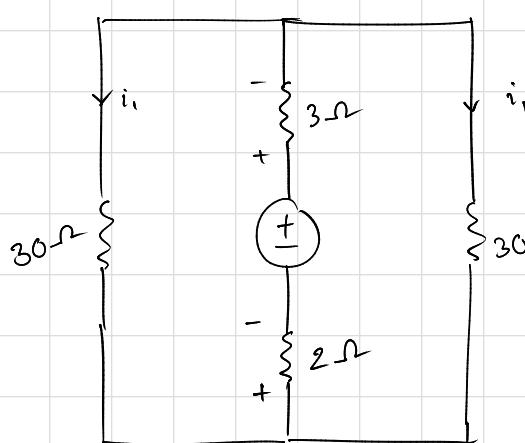
$$\therefore \text{current through } 12\Omega = 0.25A$$




$$i_2 = i_1 \times \frac{20}{20+(50+30)}$$

$$= 0.25 \times 0.2$$

$$= 0.05A$$
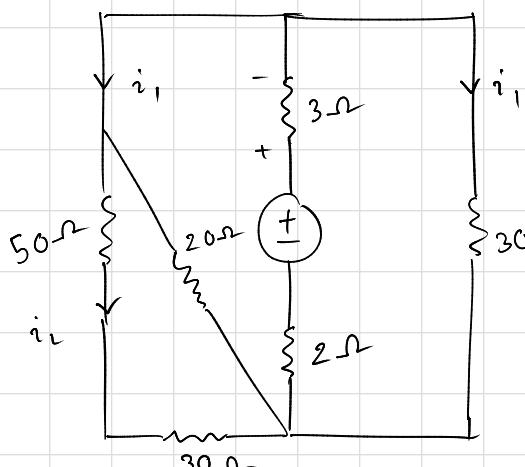
$$\therefore \text{current through } 50\Omega = 0.05A$$



$$2. a) q_1 = 20t \quad \{0 \leq t \leq 1\}$$

$$q_2 = 20 \quad \{1 \leq t < 3\}$$

$$q_3 = -\frac{40}{2}t + c = -20t + c = -20t + 80 \quad \{3 \leq t \leq 5\}$$

$$q_3(3) = q_2(3)$$

$$\Rightarrow -60 + c = 20$$

$$\Rightarrow c = 80$$

$$q_4 = \frac{40}{2}t + c = 20t + c = 20t - 120 \quad \{5 \leq t \leq 7\}$$

$$q_4(5) = q_3(5)$$

$$\Rightarrow 100 + c = -20$$

$$\Rightarrow c = -120$$

$$q_5 = 20 \quad \{7 \leq t\}$$


$$i_1 = 20$$

$$i_2 = 0$$

$$i_3 = -20$$

$$i_4 = 20$$


$$i_5 = 0$$

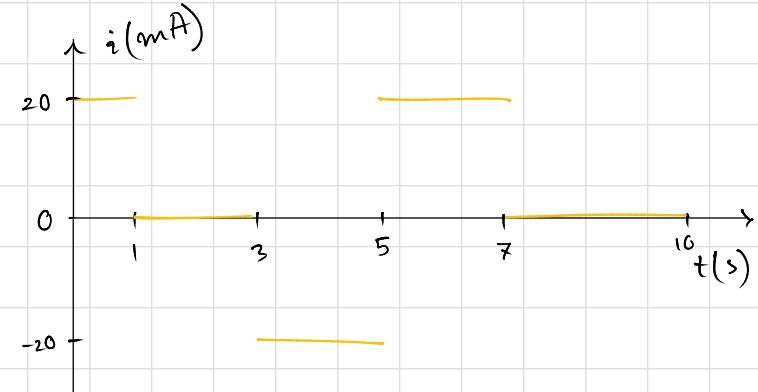

$$b) P = i^2 R$$

for $0 \leq t \leq 1$

$$P = 20^2 \times 10 = 4 \text{ mW}$$

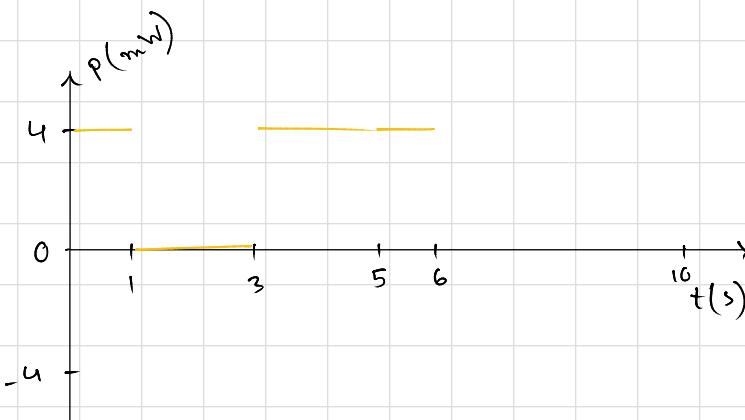

for $1 \leq t \leq 3$

$$P = 0^2 \times 10 = 0$$

total energy delivered from 0 to 6 sec


for $3 \leq t \leq 5$

$$P = (-20)^2 \times 10 = 4 \text{ mW}$$

$$E = 4 \times 1 + 0 + 4 \times 3 \\ = 16 \text{ mJ}$$

for $5 \leq t \leq 6$

$$P = 20^2 \times 10 = 4 \text{ mW}$$

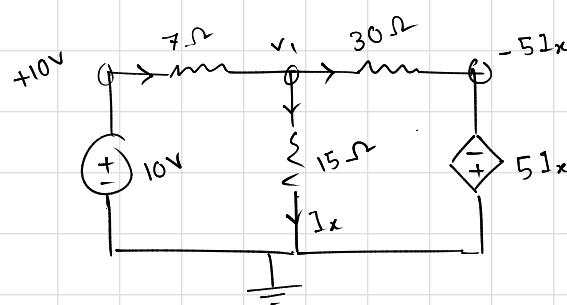

3. a)

node v_1 :

$$\frac{10 - v_1}{7} = \frac{v_1 + 5I_x}{30} + \frac{v_1}{15}$$

$$\Rightarrow \frac{10 - v_1}{7} = \frac{v_1 + \frac{5}{3}}{30} + \frac{v_1}{15} \quad [I_x = \frac{v_1}{15}]$$

$$\Rightarrow v_1 = 5.625 \text{ V} \quad \therefore I_x = 0.375 \text{ A}$$

$$\text{current through } 7\Omega = \frac{10 - v_1}{7} = 0.625 \text{ A}$$

$$\text{current through } 30\Omega = \frac{v_1 + 5I_x}{30} = 0.25 \text{ A}$$

$$\text{and } 15\Omega = I_x = 0.375 \text{ A}$$

$$\text{current through } 10\text{V} = 0.625 \text{ A}$$

$$\text{and } 5I_x = 0.25 \text{ A}$$

b) power supplied by $10V = 10 \times 0.625 = 6.25 W$

power absorbed by $7\Omega = 7 \times 0.625^2 = 2.739 W$

power absorbed by $15\Omega = 0.375^2 \times 15 = 2.109 W$

power absorbed by $30\Omega = 0.25^2 \times 30 = 1.875 W$


power supplied by $5A = 5 \times 0.375 \times 0.25 = 0.469 W$

4. a) loop 1:

$$1(i_1 + 4) + 8(i_1 - i_2) - 20 = 0$$

$$\Rightarrow i_1 + 4 + 8i_1 - 8i_2 - 20 = 0$$

$$\Rightarrow 9i_1 - 8i_2 = 16$$

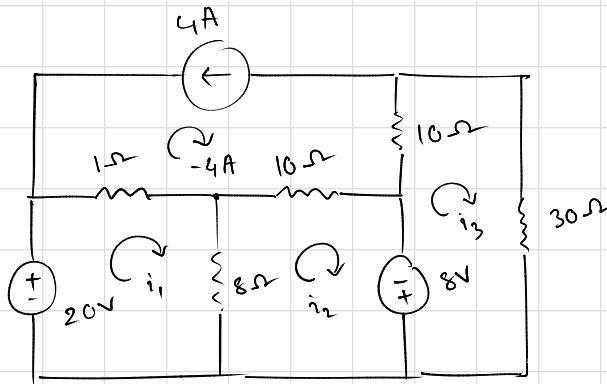

loop 2:

$$8(i_2 - i_1) + 10(i_2 + 4) - 8 = 0$$

$$\Rightarrow 8i_2 - 8i_1 + 10i_2 + 40 - 8 = 0$$

$$\Rightarrow -8i_1 + 18i_2 = -32$$

$$\begin{aligned} b) P &= i^2 R = (i_1 + 4)^2 \times 1 \\ &= 18.714 W \end{aligned}$$

loop 3:

$$10(i_3 + 4) + 30i_3 + 8 = 0$$

$$\Rightarrow 10i_3 + 40 + 30i_3 + 8 = 0$$

$$\Rightarrow 40i_3 = -48$$

$$\Rightarrow i_3 = -1.2$$

$$i_1 = 0.326 A$$

$$i_2 = -1.63 A$$

$$i_3 = -1.2 A$$

5. a) node v_1

$$3.7v_o + \frac{9i_o - v_1}{15} = 1_o$$

$$\Rightarrow 3.7(v_2 - 94) + \frac{1}{15} \left(9 \frac{v_1 - v_2}{11} - v_1 \right) = \frac{v_1 - v_2}{11}$$


$$\Rightarrow 3.7v_2 - 347.8 + \frac{1}{15} \left(\frac{9}{11}v_1 - \frac{9}{11}v_2 - v_1 \right)$$

$$= \frac{1}{11}v_1 - \frac{1}{11}v_2$$

$$\Rightarrow 3.7v_2 - 347.8 + \frac{3}{55}v_1 - \frac{3}{55}v_2 - \frac{1}{15}v_1 = -\frac{1}{11}v_1 - \frac{1}{11}v_2$$

$$\Rightarrow \left(\frac{3}{55} - \frac{1}{15} - \frac{1}{11} \right) v_1 + \left(3.7 - \frac{3}{55} + \frac{1}{11} \right) v_2 = 347.8$$
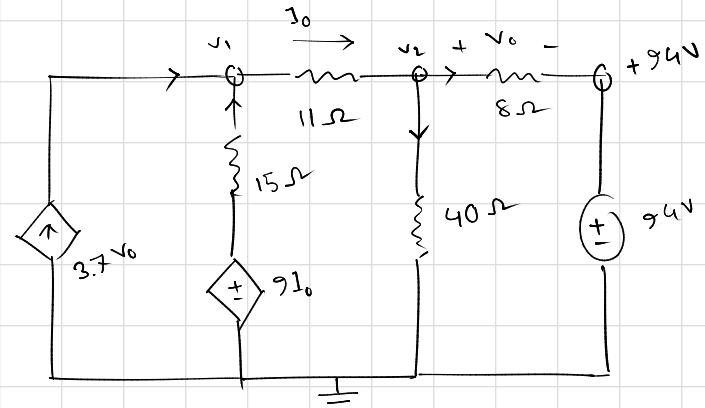
$$\Rightarrow -\frac{17}{165}v_1 + \frac{411}{110}v_2 = 347.8 \quad \text{--- (1)}$$



node v₂:

$$\frac{v_1 - v_2}{11} = \frac{v_2 - 94}{8} + \frac{v_2}{40}$$

$$\Rightarrow \frac{1}{11}v_1 - \frac{1}{11}v_2 = \frac{1}{11}v_2 - \frac{94}{8} + \frac{v_2}{40}$$

$$\Rightarrow \frac{1}{11}v_1 + \left(-\frac{1}{11} - \frac{1}{8} - \frac{1}{40} \right)v_2 = -\frac{94}{8} \quad \text{--- (ii)}$$

$$\Rightarrow \frac{1}{11}v_1 - \frac{53}{220}v_2 = -\frac{94}{8}$$

solve (i) and (ii)

$$v_1 = 126.68$$

$$v_2 = 96.578$$

b) $v_o = v_2 - 94 = 2.578$

$$I_o = \frac{v_1 - v_2}{11} = 2.74$$