
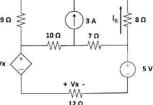


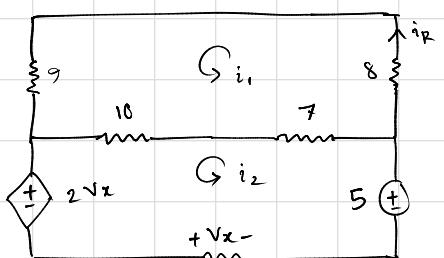Answer the following questions for the circuit shown in Figure 1:
 i) Draw the circuit with the Independent Current Source Turned Off. ii) Draw the circuit with the Independent Voltage Source Turned Off. iii) Apply the Superposition Theorem, and find the value of i_R .



current source off:



$$i_2 = \frac{v_x}{12}$$

$$\text{loop 1: } i_1(9+8+10+7) - i_2(10+7) = 0$$

$$\Rightarrow 34i_1 - \frac{17}{12}v_x = 0$$

$$\text{loop 2: } 2v_x + v_x - 5 + i_2(10+7) - i_1(10+7) = 0$$

$$\Rightarrow 3v_x - 5 + \frac{17}{12}v_x - 17i_1 = 0$$


$$\Rightarrow -17i_1 + \frac{53}{12}v_x = 5$$

$$i_1 = \frac{5}{89} \quad v_x = \frac{120}{89}$$

$$= i_R$$

$$\text{Superposition } i_R = \frac{5}{89} - \frac{2511}{1513} = -1.6034 \text{ A}$$

voltage source off:

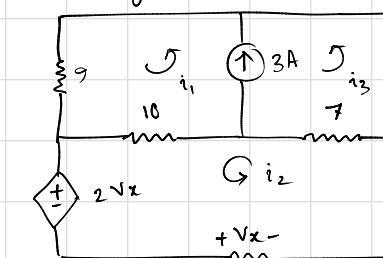

$$i_2 = \frac{v_x}{12} \quad i_1 - i_3 = 3$$

$$\text{loop 2: } 2v_x + v_x + i_2(10+7) - 10i_1 - 7i_3 = 0$$

$$\Rightarrow 3v_x + \frac{17}{12}v_x - 10(3+i_3) - 7i_3 = 0$$


$$\text{loop 1+3: } i_1(9+10) + i_3(8+7) - i_2(10+7) = 0$$

$$\Rightarrow (3+i_3)19 + 15i_3 - \frac{17}{12}v_x = 0$$


$$\Rightarrow -\frac{17}{12}v_x + 34i_3 = -57$$

$$v_x = \frac{36}{89} \quad i_3 = -\frac{2511}{1513} = i_R$$

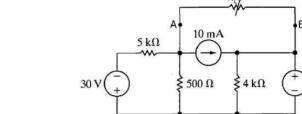
For the circuit shown in Figure 2, answer the following questions:
 i) Determine the Thevenin equivalent circuit at the A-B terminal.
 ii) For any value of R_L , what will be the maximum power delivered to this resistance?
 iii) If $R_L = 1k\Omega$, then would maximum power be achieved? If not, then what should you do to achieve maximum power?



i)

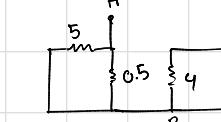
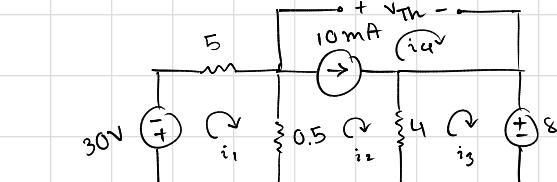
$$R_{Th} = 5 \parallel 0.5 = \frac{5}{11} k\Omega$$



$$i_4 = 0 \quad i_2 - i_4 = 10 \Rightarrow i_2 = 10$$

$$\text{loop 2+4: } v_{Th} + i_2(0.5+4) - i_1(0.5) - i_3(4) = 0$$

$$\Rightarrow v_{Th} + 4.5i_2 - 0.5i_1 - 4i_3 = 0$$

$$\Rightarrow v_{Th} + 45 - 0.5i_1 - 4i_3 = 0$$

$$\Rightarrow v_{Th} - 0.5i_1 - 4i_3 = -45$$

$$\text{loop 1: } 30 + i_1(5+0.5) - i_2(0.5) = 0$$

$$\Rightarrow 5.5i_1 - 5 + 30 = 0$$

$$\Rightarrow i_1 = \frac{-25}{5.5}$$

$$v_{Th} + 0.5 \times \frac{25}{5.5} - 4(-10) = -45$$

$$\Rightarrow v_{Th} + \frac{25}{11} + 40 = -45$$

$$\Rightarrow v_{Th} = -87.2727$$

$$\text{loop 3: } 80 + 4i_3 - 4i_2 = 0$$

$$\Rightarrow 80 + 4i_3 - 40 = 0$$


$$\Rightarrow i_3 = -10$$

$$\text{iii) } P = i^2 R_L$$

$$= \left(\frac{v_{Th}}{R_{Th} + R_L} \right)^2 \times R_L$$

$$= \left(\frac{87.2727}{454.545 + 1000} \right)^2 \times 1000$$


$$= 3.6 \text{ W}$$

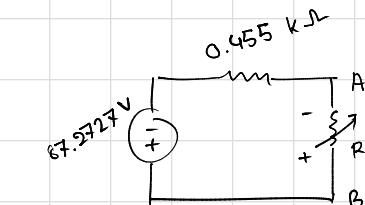

$$\text{ii) } P_{max} = \frac{v_{Th}^2}{4R_{Th}} = \frac{87.2727^2}{4 \times 0.455} \text{ mW}$$

$$= 4184.9034 \text{ mW}$$

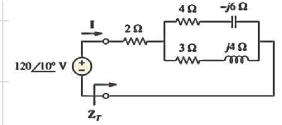Answer the following questions for the circuit shown in Figure 3:
 i) Determine Z_T . ii) Current, I. iii) Find the currents through 4Ω and 3Ω resistors.
 iv) Is the source voltage or the current, I leading in this circuit?



$$\text{i)} \quad Z_T = 2 + (4 - j6) \parallel (3 + j4)$$

$$= 6.9173 \angle 9.1026^\circ$$

$$\text{ii)} \quad I = \frac{120 \angle 10^\circ}{6.9173 \angle 9.1026^\circ} = 17.3478 \angle 0.897377^\circ$$

$$\text{iii)} \quad i_4 = I \times \frac{3 + j4}{(4 - j6) + (3 + j4)} = 11.945 \angle 9.972875^\circ$$


$$i_3 = I \times \frac{4 - j6}{(4 - j6) + (3 + j4)} = 17.183368 \angle -39.467^\circ$$

$$\text{iv)} \quad I = 17.3478 \cos(\omega t + 0.897377^\circ)$$

$$V = 120 \cos(\omega t + 10^\circ)$$

V is leading by 9.1026°

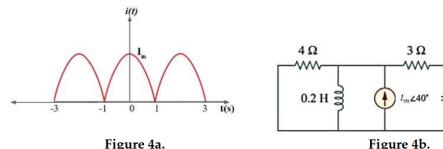For the circuit shown in Figure 4a, determine I_m if the rms value of such current is 5A. Now, determine i_o and average real power absorbed by a 3-ohm resistor using CDR in the circuit shown in Figure 4b if the angular frequency is 100 rad/s in the circuit.



$$\omega = \frac{2\pi}{2} = \pi$$

$$i(t) = I_m \cos(\pi t), -1 < t < 1$$

$$I_{rms}^2 = \frac{1}{T} \int_{-1}^1 (I_m \cos(\pi t))^2 dt$$


$$= \frac{I_m^2}{T} \frac{1}{2} \int_{-1}^1 (1 + \cos 2\pi t) dt$$

$$= \frac{I_m^2}{2T} \left\{ t \Big|_{-1}^1 + \frac{1}{2\pi} \sin 2\pi t \Big|_{-1}^1 \right\}$$

$$= \frac{I_m^2}{2T} \times 2$$

$$= \frac{I_m^2}{2}$$
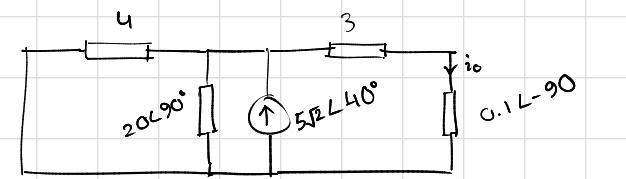
$$\Rightarrow I_m = \sqrt{2 I_{rms}^2} = 5\sqrt{2}$$



$$i_o = 5\sqrt{2} \angle 40^\circ \times \frac{(4 \parallel 20 \angle 90^\circ) + (3 + 0.1 \angle -90^\circ)}{(4 \parallel 20 \angle 90^\circ) + (3 + 0.1 \angle -90^\circ)}$$

$$= 4.0396 \angle 45.7268^\circ$$

$$P_{avg} = \frac{1}{2} i_o^2 \times R$$

$$= \frac{1}{2} i_o^2 \times 3$$

$$= 24.385$$

$$P_{avg} = \frac{1}{2} i_m^2 \times R$$

$$= \frac{1}{2} \frac{V_m^2}{R}$$