

Question 1: Answer all the questions.

(12 Marks)

- Your friend just built a circuit and connected a 300Ω bulb between a-b points as shown in Figure 1. Answer the following questions:
- Determine the Thevenin equivalent circuit for the following circuit your friend has built.
 - Determine the power absorbed by this bulb. Is the power the maximum power that can be achieved for this circuit? If not, then what should you do?
 - Now, your friend connected another bulb with a different resistance instead of the 300Ω bulb and got the same absorbed power. Determine the new resistance of this bulb.


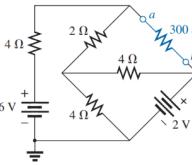
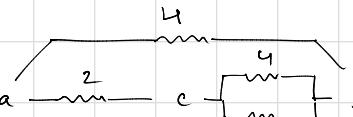


Figure 1

i)

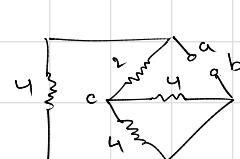

$$R_{Th} = 4 \parallel (2 + 4 \parallel 4) = 2\Omega$$


$$i_2 = 0$$

$$\text{loop 1: } i_1(4+2+4) - 2i_2 - 4i_3 - 6 = 0 \\ \Rightarrow 10i_1 - 4i_3 - 6 = 0$$

$$\text{loop 2: } i_2(4+2) - 2i_1 - 4i_3 + V_{Th} = 0 \\ \Rightarrow -2i_1 - 4i_3 + V_{Th} = 0$$

$$\text{loop 3: } i_3(4+4) - 4i_2 - 4i_1 + 2 = 0 \\ \Rightarrow -4i_1 + 8i_3 + 2 = 0$$
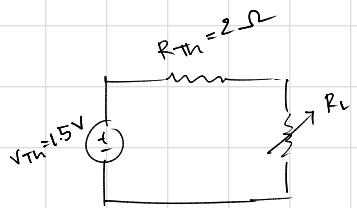
$$i_1 = \frac{5}{8}, i_3 = \frac{1}{16}, V_{Th} = \frac{3}{2}$$



ii) $R_{Th} \neq 300\Omega$


$$\text{iii) } P = \frac{V_{Th}^2}{(R_{Th} + R_L)^2} \times R_L = \frac{1.5^2}{(2 + 300)^2} \times 300 = \frac{675}{91204}$$

$$\frac{675}{91204} = \frac{V_{Th}^2}{(R_{Th} + R_L)^2} \times R_L$$

$$R_L = 0.0133\Omega$$

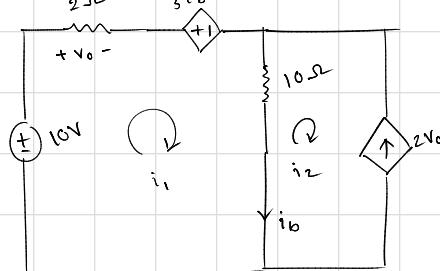Question 2: Answer all the questions.

(13 Marks)
Determine the value of V_o using the Superposition theorem for the circuit shown in Figure 2. Additionally, find the power delivered by the 10V voltage source.



$$i_1 - i_2 = i_b$$

$$i_1 = \frac{V_o}{2}, i_2 = -2V_o$$

$$\text{loop 1: } i_1(2+10) - 10i_2 - 10 + 3i_b = 0$$

$$\Rightarrow 6V_o + 20V_o - 10 + 3i_b = 0$$

$$\Rightarrow 26V_o + 3i_b = 10$$

$$\Rightarrow 26V_o + 3\left(\frac{V_o}{2} + 2V_o\right) = 10$$

$$\Rightarrow 26V_o + \frac{15}{2}V_o = 10$$

$$\Rightarrow V_o = 10 \times \frac{2}{67} = \frac{20}{67}$$

$$i_1 = \frac{V_o}{2}, i_3 = -2V_o$$

$$i_b = i_2 - i_3, i_2 - i_1 = 2$$

$$= (2+i_1) - i_3$$

$$= 2 + \frac{V_o}{2} + 2V_o = 2 + \frac{5}{2}V_o$$

loop 1+2:


$$V_o + 3i_b + 10i_2 - 10i_3 = 0$$

$$\Rightarrow V_o + 3\left(2 + \frac{5}{2}V_o\right) + 10i_b = 0$$

$$\Rightarrow V_o + 6 + \frac{15}{2}V_o + 20 + 25V_o = 0$$

$$\Rightarrow \frac{67}{2}V_o + 26 = 0$$

$$\Rightarrow V_o = -0.776$$

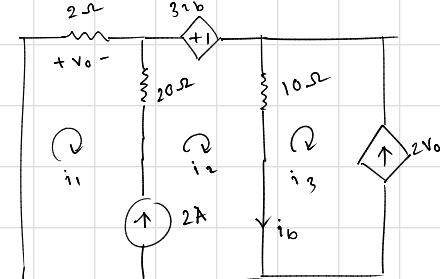

$$\text{superposition } V_o = \frac{20}{67} - 0.776 = -0.4775$$

$$P_{10V} = \frac{V_o^2}{R} = 0.04455 \text{ W}$$

Question 3: Answer all the questions

(12 Marks)

An AC current source, $i_s(t)$ [Figure 3(a)] is used in the following circuit shown in Figure 3(b). Answer the following questions:

i) Determine the equation of $i_s(t)$.

$$\text{i)} \quad i_s(t) = 4 \sin\left(\frac{2\pi}{12}t\right) = 4 \sin\left(\frac{\pi}{6}t\right)$$

$$= 4 \angle -90^\circ$$

ii) Determine the equivalent impedance of this circuit.

iii) Determine $i_o(t)$ and also by how many degrees is $i_o(t)$ leading $i_s(t)$?

$$\text{ii)} \quad X = a \parallel b \parallel (c+d)$$

$$= 0.105244 \angle 88.44389^\circ$$

$$\text{iii)} \quad i_o = i \times \frac{a \parallel b}{(c+d) + (a \parallel b)}$$

$$= 0.02177 \angle 79.5168^\circ$$

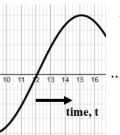


Figure 3(a)



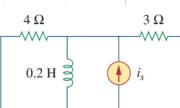


Figure 3(b)

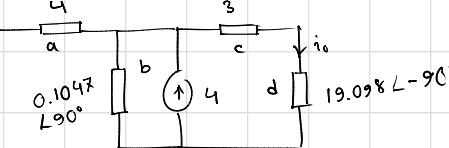
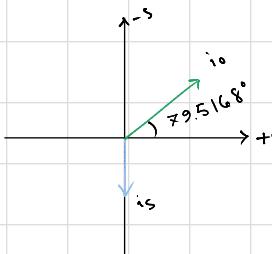
$$i_o(t) = 0.02177 \cos\left(\frac{\pi}{6}t + 79.5168^\circ\right)$$



$$i_o(t) \text{ is leading } i_s(t) \text{ by } 90^\circ + 79.5168^\circ = 169.5168^\circ$$

When the voltage waveform of Figure 4(a) is applied across a 2 ohm resistor, the average power absorbed by the resistor is 4.267 W. Another AC circuit is shown in Figure 4(b). Now answer the following questions:

i) Find the rms value, v_{rms} of the voltage waveform shown in Figure 4(a).

$$\text{ii)} \quad v(t) = \begin{cases} \frac{v_m}{2}t, & 0 < t < 2 \\ 0, & 2 < t < 5 \end{cases}$$

$$\int_0^5 v(t)^2 dt = \int_0^2 \frac{v_m^2}{4} t^2 dt + \int_2^5 0^2 dt$$


$$= \frac{v_m^2}{12} t^3 \Big|_0^2 = \frac{2}{3} v_m^2$$

$$v_{rms}^2 = \frac{1}{T} \int_0^5 v(t)^2 dt = \frac{1}{5} \times \frac{2}{3} v_m^2 = \frac{2}{15} v_m^2$$

$$\frac{v_{rms}^2}{2} = 4.267 \Rightarrow v_{rms}^2 = 8.534$$

$$\Rightarrow v_m^2 = 8.534 \times \frac{15}{2} = 64.005$$

$$\Rightarrow v_m = 8 V$$

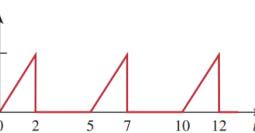

iii) Use this rms [from ii)] value as the maximum amplitude of the sinusoidal voltage source in the circuit shown in Figure 4(b). Determine $I_o(t)$, and average power absorbed by the 30 ohm resistor in the circuit.

$$\text{iii)} \quad X = a + (b+c) \parallel (d+e)$$

$$= 42.022 \angle -3.3274^\circ$$

$$I = \frac{V}{X} = 0.069487 \angle 48.3274^\circ$$


$$I_o = I \times \frac{d+e}{(b+c) + (d+e)}$$

$$= 0.0485 \angle 60.422^\circ$$

$$I_o(t) = 0.0485 \cos\left(\frac{2\pi}{5}t + 60.422^\circ\right)$$

$$i_{rms} = \frac{0.0485}{\sqrt{2}} = 0.0343$$

$$P = i_{rms}^2 \cdot 30 = 0.03533 W$$

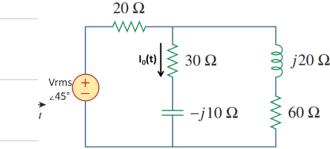

$$V = 2.92 \angle 45^\circ$$

