
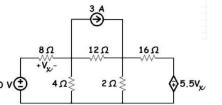


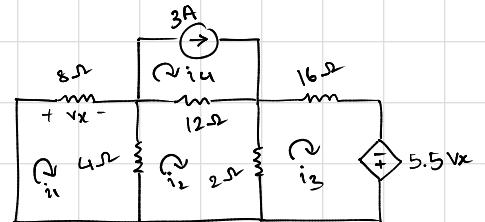Use the superposition theorem to determine the value of  $V_x$  for the circuit shown in Figure 1. Also, the 8-ohm resistor absorbs power from both independent sources. Analyze the circuit and determine which independent source in this circuit supplies most of the power to the 8-ohm resistor.



voltage source off



$$i_1 = \frac{v_x}{8} \quad i_4 = 3$$


$$\text{loop 1: } v_x + 4i_1 - 4i_2 = 0 \\ \Rightarrow v_x + \frac{1}{2}v_x - 4i_2 = 0 \\ \Rightarrow \frac{3}{2}v_x - 4i_2 = 0$$

$$\text{loop 2: } i_2(4+12+2) - 4i_1 - 12i_4 - 2i_3 = 0 \\ \Rightarrow 18i_2 - \frac{1}{2}v_x - 36 - 2i_3 = 0 \\ \Rightarrow -\frac{1}{2}v_x + 18i_2 - 2i_3 = 36$$

$$\text{loop 3: } -5.5v_x + i_3(16+2) - 2i_2 = 0 \\ \Rightarrow -5.5v_x - 2i_2 + 18i_3 = 0$$

$$v_x = 6.48 \quad i_2 = 2.43 \quad i_3 = 2.25$$

current source off

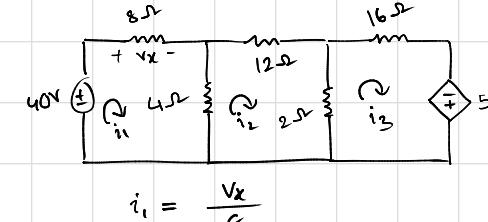

$$i_1 = \frac{v_x}{8}$$

$$\text{loop 1: } -40 + v_x + 4i_1 - 4i_2 = 0$$

$$\Rightarrow v_x + \frac{1}{2}v_x - 4i_2 = 40 \\ \Rightarrow \frac{3}{2}v_x - 4i_2 = 40$$

$$\text{loop 2: } i_2(4+2+12) - 4i_1 - 2i_3 = 0$$

$$\Rightarrow -\frac{1}{2}v_x + 18i_2 - 2i_3 = 0$$

$$\text{loop 3: } -5.5v_x - 2i_2 + 18i_3 = 0$$

$$v_x = 32 \quad i_2 = 2 \quad i_3 = 10$$

$$\text{Superposition } v_x = 32 + 6.48 = 38.48 \text{ V}$$



$$\text{power current source} = \frac{6.48^2}{8} = 5.2488 \text{ W}$$

$$\text{power voltage source} = \frac{32^2}{8} = 128 \text{ W}$$

voltage source supplies most of the power.


For the circuit shown in Figure 2, answer the following questions:

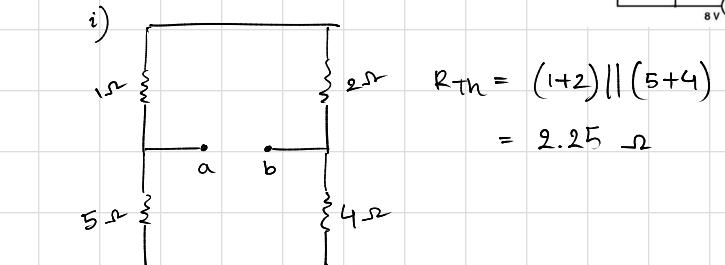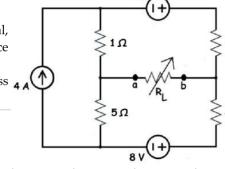- Determine the Thevenin equivalent circuit at the a-b terminal.
- Suppose your friend suggests that if you connect a 20V-40W bulb across a-b terminal, then you will get maximum bulb intensity. Is he right? If not, then calculate the resistance of the bulb that would get maximum intensity.
- Determine the maximum power delivered to the bulb that would be connected across the a-b terminal.



$$R_{Th} = (1+2) \parallel (5+4)$$

$$= 2.25 \Omega$$

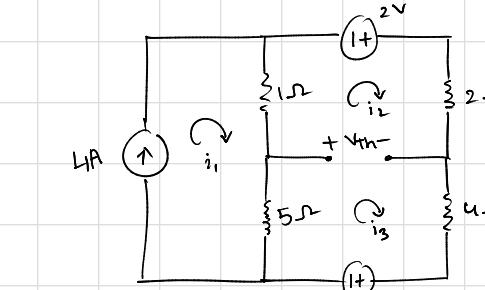


$$i_1 = 4 \quad i_3 - i_2 = 0$$

$$\text{loop 2: } -v_{Th} - 2 + i_2(1+2) - i_1 = 0 \\ \Rightarrow -v_{Th} + 3i_2 = 6$$

$$\text{loop 3: } v_{Th} + 8 + i_3(4+5) - 5i_1 = 0 \\ \Rightarrow v_{Th} + 8 + 9i_2 - 20 = 0 \\ \Rightarrow v_{Th} + 9i_2 = 12$$

$$v_{Th} = -1.5 \quad i_2 = 1.5$$

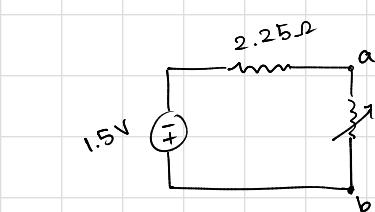


ii)  $P = \frac{V^2}{R} \Rightarrow 40 = \frac{20^2}{R} \Rightarrow R = 10 \Omega$

the resistance of the bulb should be  $= R_{Th} = 2.25 \Omega$

For the circuit shown in Figure 3, where  $v_g(t) = 247.49 \cos(1000t + \pi/4)$

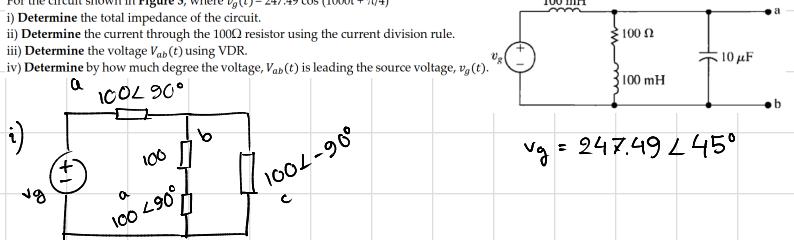- i) Determine the total impedance of the circuit.
- ii) Determine the current through the  $100\Omega$  resistor using the current division rule.
- iii) Determine the voltage  $V_{ab}(t)$  using VDR.
- iv) Determine by how much degree the voltage,  $V_{ab}(t)$  is leading the source voltage,  $v_g(t)$ .



$$Z = 100 L 90^\circ + (100 + 100 L 90^\circ) \parallel 100 L -90^\circ$$

$$= 100$$

$$\text{i)} i = \frac{v_g}{Z} = 2.4749 L 45^\circ$$

$$i(100\Omega) = i \times \frac{100 L -90^\circ}{100 + 100 L 90^\circ + 100 L -90^\circ}$$

$$= 2.4749 L -45^\circ$$


$$\text{ii)} v_{ab} = v_g \times \frac{(100 + 100 L 90^\circ) \parallel 100 L -90^\circ}{100 L 90^\circ + (100 + 100 L 90^\circ) \parallel 100 L -90^\circ}$$

$$= 350.0037$$


$$v_{ab}(t) = 350.0037 \cos(1000t)$$

$$\text{iv)} v_g(t) = 247.49 \cos(1000t + 45^\circ)$$
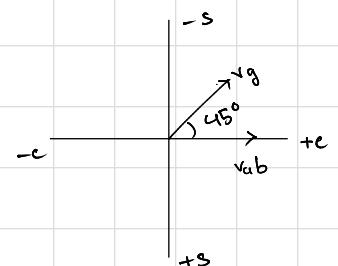
$$v_{ab}(t) \text{ is leading by } 360^\circ - 45^\circ \\ = 315^\circ$$



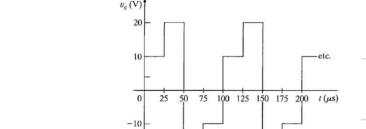i) Calculate the rms value of the periodic voltage shown in Figure 4a.



$$\int_0^{100} v(t)^2 dt \\ = \int_0^{25} 10^2 dt + \int_{25}^{50} 20^2 dt + \int_{50}^{75} 20^2 dt + \int_{75}^{100} 10^2 dt \\ = 10^2 \times 25 + 20^2 \times 25 + 20^2 \times 25 + 10^2 \times 25 = 25000$$

$$v_{rms} = \sqrt{\frac{1}{100} \times 25000} = 15.81139$$

ii) Now, use this rms value as the maximum amplitude of the sinusoidal voltage source in the circuit shown in Figure 4b. Determine  $I_o(t)$  and average real power absorbed by the  $2\Omega$  resistor in the circuit. The angular frequency is  $100 \text{ rad/s}$  in the circuit.


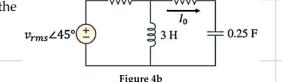


Figure 4b

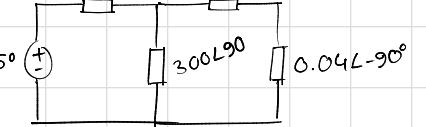

$$Z = 1 + 300 L 90^\circ \parallel (2 + 0.04L -90^\circ)$$

$$= 3.000563 L -0.5092^\circ$$

$$i = \frac{v}{Z} = 5.26947 L 45.509^\circ$$

$$i_o = i \times \frac{300 L 90^\circ}{300 L 90^\circ + 2 + 0.04L -90^\circ}$$

$$= 5.27 L 45.89^\circ$$

$$i_o(t) = 5.27 \cos(100t + 45.89^\circ)$$

$$i_{rms} = \frac{i_o}{\sqrt{2}} = \frac{5.27}{\sqrt{2}} = 3.72649$$

$$P_{avg} = i_{rms}^2 \times R = 3.72649^2 \times 2 = 27.7735 \text{ W}$$