


$$(1) \text{ i) slope}_{0,1} = \frac{-5}{1} = -5$$

$$\text{slope}_{1,2} = \frac{5}{1} = 5$$

$$\text{slope}_{2,3} = \frac{4}{1} = 4$$

$$\text{slope}_{3,4} = 0$$

$$\text{slope}_{4,5} = 0$$

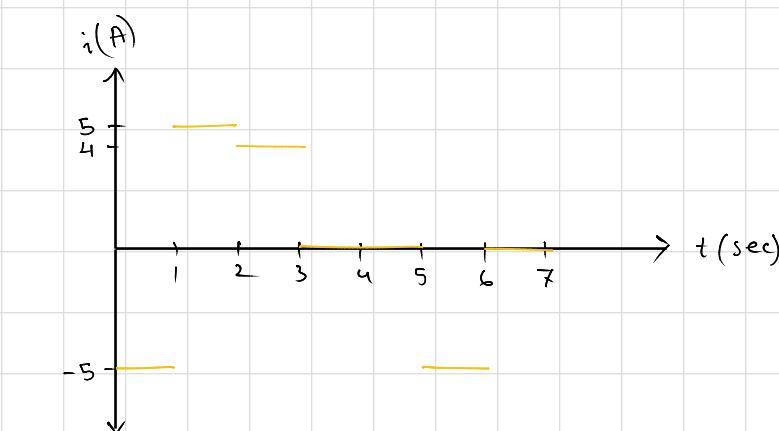

$$i(2.5) = 4 \text{ A}$$

$$i(5.5) = -5 \text{ A}$$


$$\text{slope}_{6,7} = 0$$

ii)  $P = i^2 R$  therefore  $P$  is maximum when  $i$  is maximum


In the graph  $i_{\max} = 5 \text{ A}$  from  $t = 1 \text{ s}$  to  $t = 2 \text{ s}$

$$\therefore P_{\max} = 5^2 \times 20 = 500 \text{ W}$$
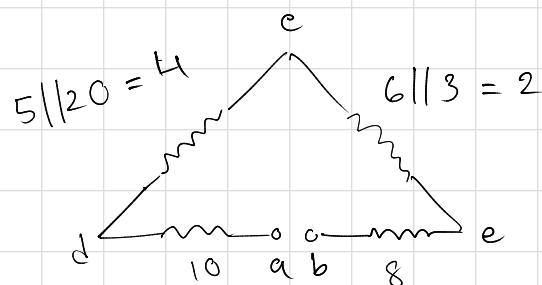
$$(2) \text{ i) } \text{eqv}_{ab} = 24 \Omega$$



$$4+10+8+2 = 24$$

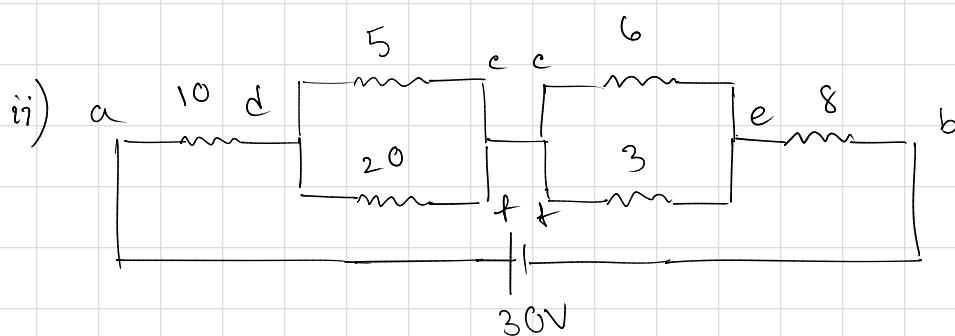

$$i_{ab} = \frac{30}{24} = 1.25 \text{ A}$$

$$\therefore i_{eb} = 1.25 \text{ A}$$

$$i_{ce} = 1.25 \times \frac{3}{3+6} = 0.4167$$

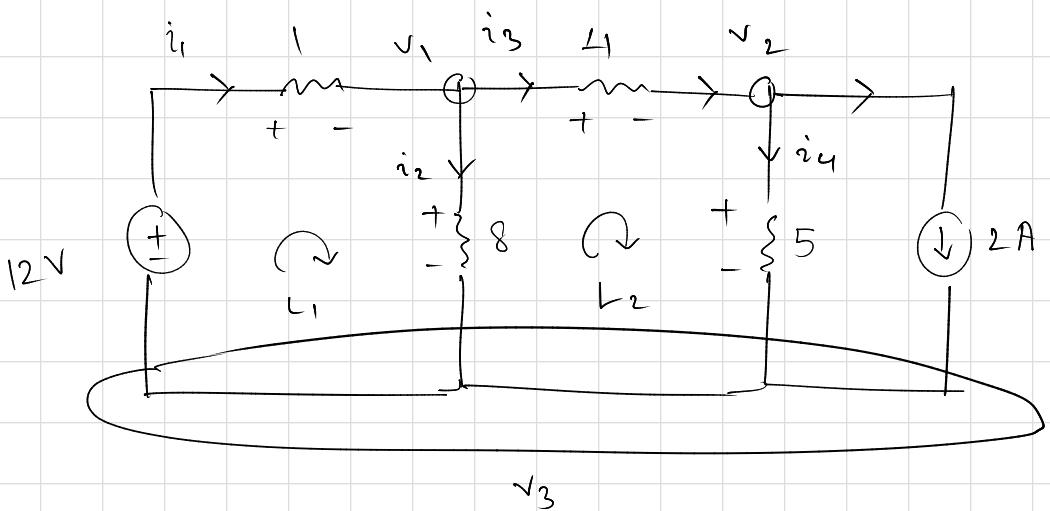
(3)

loop 1

$$i_1 + 8i_2 - 12 = 0$$

$$\Rightarrow i_1 + i_3 + 8i_2 - 12 = 0$$

$$\Rightarrow 9i_2 + i_3 - 12 = 0$$

loop 2

$$4i_3 + 5i_4 - 8i_2 = 0$$

$$\Rightarrow 4i_3 + 5i_3 - 10 - 8i_2 = 0 \quad [i_4 = i_3 - 2]$$

$$\Rightarrow -8i_2 + 9i_3 - 10 = 0$$

$$i_2 = 1.1 \text{ A} \quad i_3 = 2.09 \text{ A}$$

$$i_1 = 1.1 + 2.09 = 3.19 \text{ A}$$

$$i_4 = 2.09 - 2 = 0.09 \text{ A}$$

$$i_1 = \frac{12 - v_1}{1} \Rightarrow v_1 = 12 - 3.19 = 8.81 \text{ V}$$

$$i_2 = \frac{v_1 - v_3}{8} \Rightarrow v_3 = v_1 - 8i_2$$

$$= 8.81 - 8 \times 1.1$$

$$= 0 \text{ V}$$

$$i_3 = \frac{v_1 - v_2}{4} \Rightarrow v_2 = v_1 - 4i_3$$

$$= 8.81 - 4 \times 2.09$$

$$= 0.45 \text{ V}$$

(c)

loop 1:

$$120 + 30i_1 + 10(i_1 - i_3) = 0$$

$$\Rightarrow 120 + 30i_1 + 10(i_1 + 3i_0) = 0$$

$$\Rightarrow 120 + 30i_1 + 10i_1 - 15i_2 = 0$$

$$\Rightarrow 40i_1 - 15i_2 = -120$$

loop 2:


$$-120 + 10(i_2 - i_3) + 30i_2 = 0$$

$$\Rightarrow 10(i_2 + 3i_0) + 30i_2 = 120$$

$$\Rightarrow 10\left(i_2 - \frac{3}{2}i_2\right) + 30i_2 = 120$$

$$\Rightarrow 10i_2 - 15i_2 + 30i_2 = 120$$
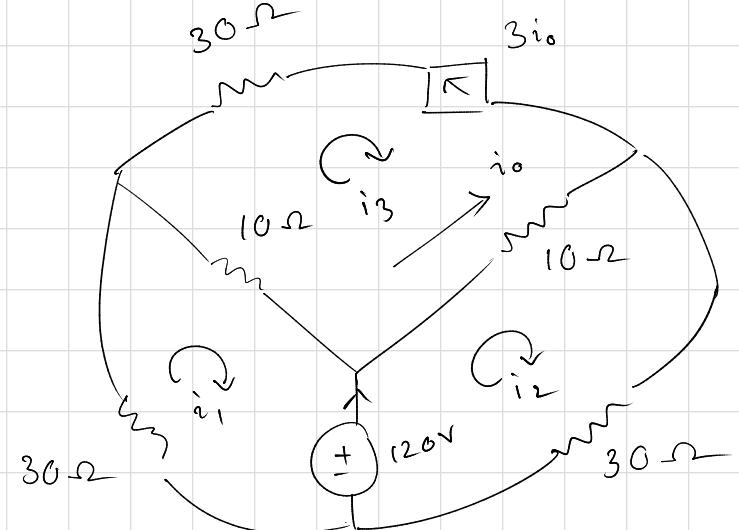
$$\Rightarrow i_2 = \frac{120}{25} = 4.8 \text{ A}$$



$$i_0 = i_2 - i_3 = i_2 + 3i_0$$

$$\Rightarrow 2i_0 = -i_2$$

$$\Rightarrow i_0 = -\frac{i_2}{2}$$

$$i_0 = -2.4 \text{ A}$$

current through the battery

$$i_2 - i_1 = 4.8 + 1.2 = 6 \text{ A}$$


$$\therefore i_1 = \frac{-120 + 15i_2}{40}$$

$$= \frac{-120 + 72}{40}$$

$$= -1.2 \text{ A}$$

5

i) at the node with  $v_2$  voltage

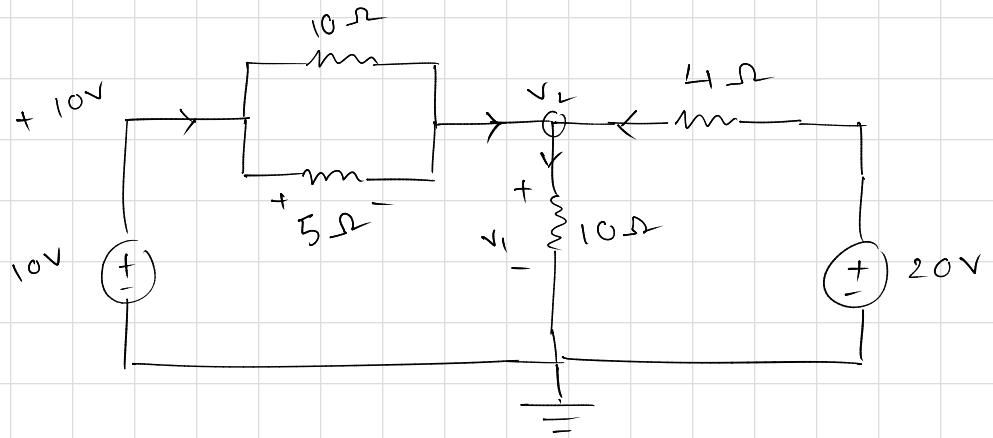

$$\frac{10 - v_2}{10/15} + \frac{20 - v_2}{4} = \frac{v_2}{10}$$

$$\Rightarrow \frac{3}{10} (10 - v_2) + \frac{20 - v_2}{4} = \frac{v_2}{10}$$

$$\Rightarrow 6(10 - v_2) + 5(20 - v_2) = 2v_2$$

$$\Rightarrow 13v_2 = 160$$

$$\Rightarrow v_2 = 12.308$$

$$v_1 = v_2 - 0 = 12.308 \text{ V}$$

$$\begin{aligned} \text{current in } 5\Omega, i &= \frac{10 - v_2}{5} \\ &= \frac{10 - 12.308}{5} \\ &= -0.46 \text{ A} \end{aligned}$$

ii) current through  $4\Omega$  resistor

$$\begin{aligned} i_1 &= \frac{20 - v_2}{4} \\ &= \frac{20 - 12.308}{4} \\ &= 1.923 \text{ A} \end{aligned}$$

therefore 1.923 A current is

$$P = vi = 20 \times 1.923 = 38.46 \text{ W}$$

flowing out of the positive

terminal of 20V voltage source,

meaning it is supplying power.